

PHY103 MOST LIKELY DEFENSE QUESTIONS

COMPILED
BY
ROWLAND
08163641878

QUESTIONS ON ELECTRICITY:

1. Define EMF of a cell

EMF of a cell can be defined as the total work done in driving one Coulomb of electricity round a circuit.

It can also be defined as the potential difference between the terminals of a cell when it is an open circuit (a circuit not delivering current to an external resistor)

Mathematically

$$EMF = I(R + r)$$

2. State Ohm's law

Ohm's law states that the current flowing through a metallic conductor is directly proportional to the potential difference across its ends provided temperature and other physical conditions remain constant.

Mathematically,

$$V = IR$$

3. Write short note on the following:

a) Resistance b) Current c) Potential difference.

RESISTANCE:

Resistance is the opposition offered to the flow of current. Generally, conductors have a lesser resistance compared to insulators and will therefore allow easy passage of current through them. Resistance is measured in ohms (Ω)

CURRENT:

Current is the flow of charges with respect to time. It is measured in Ampere. Mathematically,


$$\text{Current (I)} = \frac{\text{Charge (Q)}}{\text{time (t)}}$$

POTENTIAL DIFFERENCE:


Potential difference is the work done in moving a unit charge from one point to another in an electric circuit.

4. Identify the following Symbols:

 : Resistor


 : Rheostat Resistor


 : Ammeter


 : Voltmeter


 : Capacitor

 : Cell

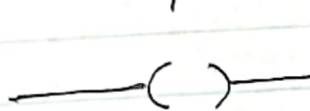
 : Key (Open circuit)

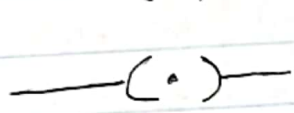
 : Key (Closed circuit)


 : Galvanometer

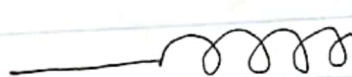 : Inductor

 : Resistor

 : Rheostat resistor

 : A.C. Circuit

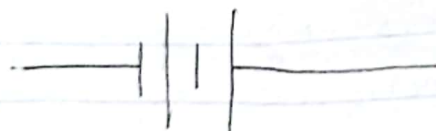 : Battery

5. Differentiate between ~~primary~~ Primary Cells & Secondary Cells

Primary Cells are cells in which current is produced as a result of non-reversible chemical changes within the cell. Primary Cells are non-rechargeable.

Examples of Primary Cells are:

- a) Daniel Cell
- b) Leclanche' Cell (Wet & Dry type)

Secondary cells are cells in which the chemical action that produce current can be reversed. They are also called Accumulators. They are rechargeable. Examples are:

- a) Lead Acid Accumulator
- b) Nickel Iron Accumulator

6) Differentiate between Cell and Battery

A Cell is a single unit of a device which converts chemical energy to electrical energy.

A battery is a collection of cells which converts chemical energy to electrical energy

7) Differentiate between Lost voltage and Terminal P.D.

Lost voltage is the voltage across internal resistance of a cell. Internal resistance of the cell is the opposition to the flow of current inside the cell.

Terminal Potential Difference is defined as the potential difference between the terminals of a cell when it is delivering current to an external resistance.

8) Differentiate between Ohmic & Non-Ohmic materials with examples.

Ohmic materials are materials which obey Ohm's law or work based on the principle of Ohm's Law. Examples: Metals and Resistors.

9) Non-Ohmic materials are materials which do not obey Ohm's Law. Example: diodes and Semiconductors

10) ~~What~~ are the State factors that can affect the Resistance of a Conductor


- Length of Conductor
- Area of Conductor
- Temperature
- Type of material or Substance

11) State methods of measuring resistance

- Wheatstone bridge method
- Potentiometer
- Ammeter-Voltmeter method

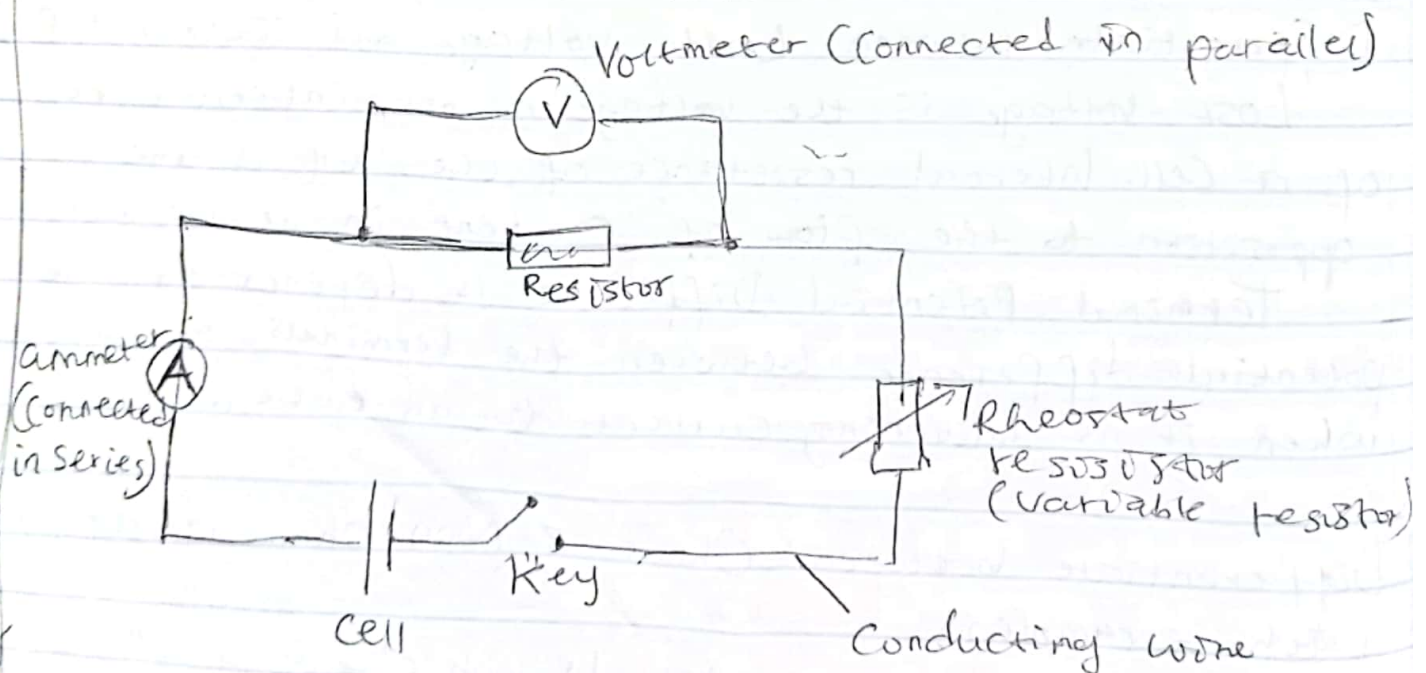12) CONNECTION OF VOLTMETER & AMMETER IN A CIRCUIT

- Voltmeters are usually connected in parallel in a circuit. This is because they have high resistance.
- Ammeters are connected in series in a circuit. This is because it has a low resistance and will not alter the current it measures.



13. GALVANOMETER-AMMETER CONVERSIONS

To convert a galvanometer to Ammeter, a low resistance shunt is connected in parallel with the galvanometer.

~~It~~

14. GALVANOMETER-VOLTMETER CONVERSIONS

To convert a galvanometer to a voltmeter, a high resistance multiplier is connected in series with the galvanometer.

OPTICS

1. Write short notes on the following:

- Ⓐ Critical angle Ⓑ Snell's Law Ⓒ Refraction Ⓓ Reflection
- Ⓔ Laws of Reflection Ⓕ Total Internal Reflection.

CRITICAL ANGLE:

Critical angle is the angle of incidence when the angle of refraction is 90° .

SNELL'S LAW:

Snell's law states that the ratio of sine of angle of incidence to sine of angle of refraction for any given medium is a constant known as Refractive index.

Mathematically, $n = \frac{\sin i}{\sin r}$

REFRACTION:

Refraction is the change in direction, speed and wavelength of a wave as it moves from one medium to another.

REFLECTION:

Reflection is also a property of wave by which a wave hits an object and bounces off it.

LAWS OF REFLECTION:

- a) The incident ray, reflected ray and the normal lie on the same plane.
- b) The angle of incidence and angle of reflection are equal.

TOTAL INTERNAL REFLECTION:

Total internal reflection is the complete reflection of an incident ray of light when the angle of incidence in the denser medium exceeds the critical angle.

Note - For total internal reflection to occur, light must travel from an optically denser medium to an optically less dense medium.

LAWS OF REFRACTION

1. a) The incident ray, refracted ray and normal all lie on the same plane.
- b) The ratio of sine of angle of incidence to sine of angle of refraction equals a constant known as relative index.

2.) Outline the characteristics of images formed by a plane mirror

- a) Image is the same size as object
- b) Image is virtual
- c) Image is laterally inverted
- d) Image is far behind the mirror as object is in front of the mirror.
- e) Image is upright.

3.) Write Short note on the following:

a) Pole (b) Principal Focus (c) Focal length

Pole:

Pole is the center of the reflecting surface of curved mirrors.

Principal Focus:

Principal focus is the point where rays of light converge or appear to ~~div~~ diverge from after reflection.

Focal length:

Focal length is the distance between the principal focus and reflecting surface of a curved mirror.